

Course: B. Tech. Branch :Electronics Engineering Semester : V

Subject Code & Name: (BTEXOE505A) Digital System Design

Max Marks: 60

Date:10-01-24


Duration: 3 Hr.

Instructions to the Students:

1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

(Level/CO) Marks

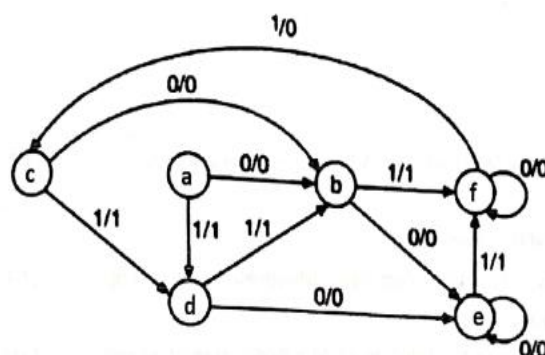- Q. 1 Solve Any Two of the following.** 12
- A) Explain the following data objects with syntax in VHDL File, signal, Variable, file. CO4 6
- B) Explain the various data types in VHDL. CO4 6
- C) Write different types of delays used in VHDL. CO4 6
- Q.2 Solve Any Two of the following.** 12
- A) What is subprogram? Explain 'Function' and 'Procedure' with their syntax. CO4 6
- B) What is the purpose of test bench in VHDL? Design Half Adder and write test bench code. CO1, CO4 6
- C) Describe the concepts of component declaration and instantiation with suitable example. CO1, CO4 6
- Q. 3 Solve Any Two of the following.** 12
- A) Design half-subtractor and Write a VHDL code using behavioral modeling. CO1 6
- B) Design 3:8 decoder and write VHDL code using structural modeling. CO2 6
- C) Design a full-adder using two half-adders and write VHDL code for it. CO1 6
- Q.4 Solve Any Two of the following.** 12
- A) Define FSM. Also Differentiate between Mealy and Moore machines. CO3 6
- B) Reduce the following state diagram and prepare a state table for reduced state diagram. CO3 6



C) Draw the Melay state diagram for sequence detector 1001 and 0110. **CO3** **6**

Q. 5 Solve Any Two of the following. **12**

A) Explain the following terms in details **CO3** **6**

- i. Clock skew
- ii. Dynamic Hazards
- iii. PLD

B) Explain Metastability and Synchronizers. **CO3** **6**

C) Briefly explain the architecture of a Complex Programmable Logic Device **CO4** **6**

***** End *****