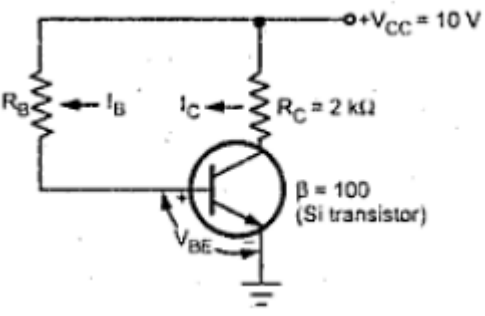
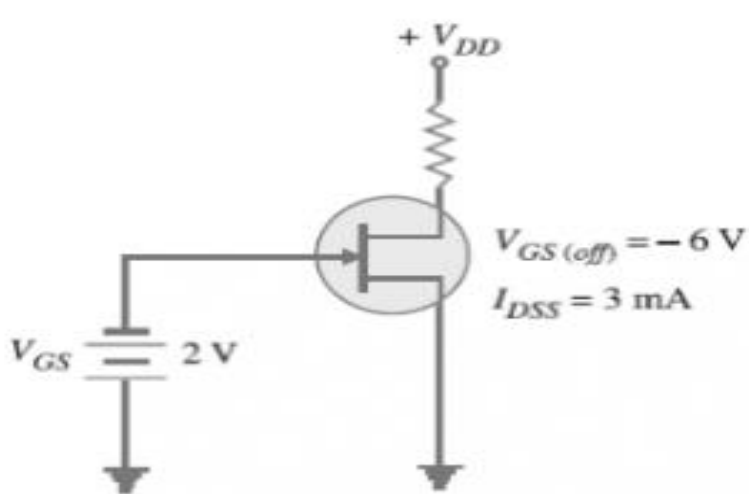
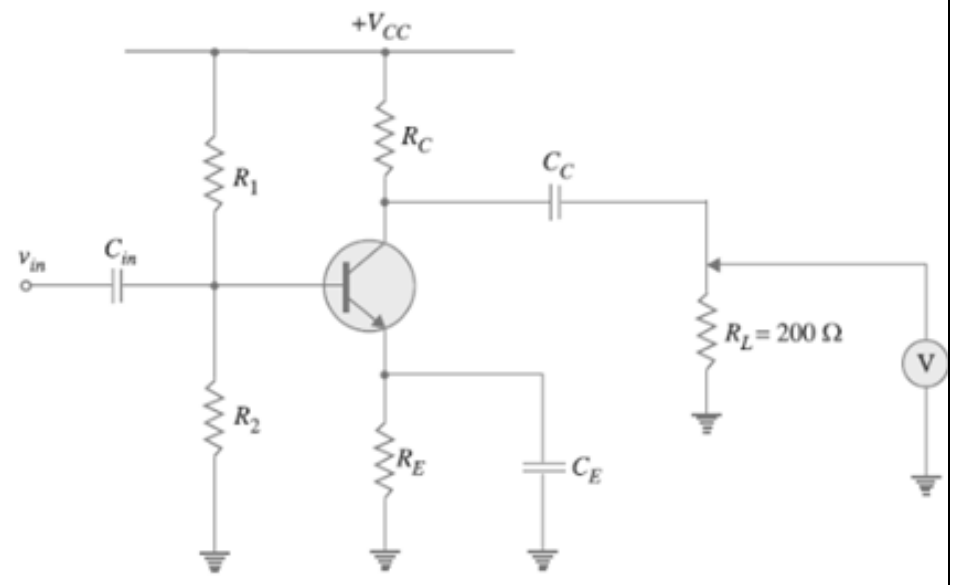


<b>DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE</b> <b>Winter Examination – 2023</b> <b>Course: B. Tech.                      Branch: E&amp;TC                      Semester: III</b> <b>Subject Code &amp; Name BTEXC302&amp; Electronic Devices &amp; Circuits</b> <b>Max Marks: 60                      Date:11/03/2023                      Duration: 2:00 To 5:00 PM</b>			
<b>Instructions to the Students:</b> 1. All the questions are compulsory. 2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in ( ) in front of the question. 3. Use of non-programmable scientific calculators is allowed. 4. Assume suitable data wherever necessary and mention it clearly.			
		Level/(CO)	Marks
<b>Q. 1</b>	<b>Solve Any Two of the following.</b>		<b>12</b>
<b>A)</b>	<b>Derive the relation between <math>\alpha</math> &amp; <math>\beta</math> with respect to BJT.</b>	<b>C01</b>	<b>6</b>
<b>B)</b>	<b>In the circuit shown below, for <math>R_B=300K\Omega</math> and <math>R_C=150K\Omega</math> calculate <math>I_B</math>, <math>I_C</math> and <math>V_{CE}</math>?</b> 	<b>C03</b>	<b>6</b>
<b>C)</b>	<b>Draw neat diagram of RC Coupled amplifier and explain in detail.</b>	<b>C03</b>	<b>6</b>
<b>Q.2</b>	<b>Solve Any Two of the following.</b>		<b>12</b>
<b>A)</b>	<b>Explain E-MOSFET in detail.</b>	<b>C03</b>	<b>6</b>
<b>B)</b>	<b>What is CMOS inverter? Explain its transfer characteristics.</b>	<b>C01</b>	<b>6</b>
<b>C)</b>	<b>Determine the value of drain current for the circuit shown in Fig.</b>	<b>C03</b>	<b>6</b>

			
<b>Q. 3</b>	<b>Solve Any Two of the following.</b>		<b>12</b>
<b>A)</b>	<b>Explain class c power amplifier in detail.</b>	<b>C02</b>	<b>6</b>
<b>B)</b>	<b>Determine the a.c. load power for the circuit shown in fig</b>	<b>C03</b>	<b>6</b>
			
<b>C)</b>	<b>Derive Expression for Maximum Efficiency of Class B Power Amplifier.</b>	<b>C02</b>	<b>6</b>
<b>Q.4</b>	<b>Solve Any Two of the following.</b>		<b>12</b>
<b>A)</b>	<b>What are the four different types of feedback amplifier? Explain in detail.</b>	<b>C04</b>	<b>6</b>
<b>B)</b>	<b>The overall gain of a multistage amplifier is 140. When negative voltage feedback is applied, the gain is reduced to 17.5. Find the fraction of the output that is feedback to the input.</b>	<b>C04</b>	<b>6</b>
<b>C)</b>	<b>Explain the principle of positive feedback.</b>	<b>C04</b>	<b>6</b>

<b>Q. 5</b>	<b>Solve Any Two of the following.</b>		<b>12</b>
<b>A)</b>	<b>Draw a neat diagram of clapp oscillator &amp; explain in detail.</b>	<b>C01</b>	<b>6</b>
<b>B)</b>	<b>1 mH inductor is available. Choose the capacitor values in a Colpitts oscillator so that <math>f = 1</math> MHz and feedback factor equal to 0.25</b>	<b>C04</b>	<b>6</b>
<b>C)</b>	<b>i)State Barkhausen criterion for sustained oscillation. ii)Differentiate oscillator from amplifier.</b>	<b>C04</b>	<b>6</b>
	<b>*** End ***</b>		

**The grid and the borders of the table will be hidden before final printing.**